

## EE2703 week4

G.Sai Krishna Reddy <ee21b049>

March 2, 2023

### 1 Sorting in topological order:

```
[85]: import networkx as nx

# Create an empty directed acyclic graph (DAG)
g = nx.DiGraph()

# Read the netfile and add nodes and edges to the graph
filename = "c17.net"
try:
    with open(filename) as f:
        for line in f:
            parts = line.strip().split()
            if len(parts) < 4:
                raise ValueError("Invalid line: " + line)
            gate_id, gate_type, *inputs, output = parts
            g.add_node(output, gate_type=gate_type)
            for input_node in inputs:
                g.add_edge(input_node, output)
except FileNotFoundError:
    print("Error: File not found:", filename)
    exit(1)
except ValueError as e:
    print("Error:", e)
    exit(1)

# Get the topological order of the nodes
try:
    topological_order = list(nx.topological_sort(g))
    print(topological_order)
except nx.exception.NetworkXUnfeasible:
    print("Error: Graph contains a cycle or graph changed during iteration, so
    the circuit can't be evaluated.")
```

```
['N2', 'N7', 'N1', 'N3', 'N6', 'n_0', 'n_1', 'n_3', 'n_2', 'N22', 'N23']
```

## 2 Logic Gates:

```
[86]: def evaluate_gate(gate_type, input_states):
    if gate_type == "and2":
        return int(all(input_states))
    elif gate_type == "or2":
        return int(any(input_states))
    elif gate_type == "xor2":
        return int(sum(input_states) % 2 == 1)
    elif gate_type == "nand2":
        return int(not all(input_states))
    elif gate_type == "nor2":
        return int(not any(input_states))
    elif gate_type == "xnor2":
        return int(sum(input_states) % 2 == 0)
    elif gate_type == "inv":
        return int(not input_states[0])
    elif gate_type == "buf":
        return int(input_states[0])
    else:
        raise ValueError(f"Invalid gate type: {gate_type}")
```

## 3 Evaluation of the circuit using topological order:

```
[87]: # Read the list of input vectors
import time
start_time = time.time()
def f(filename):

    inputs = []
    with open(filename) as f:

        inputs=f.readlines()
        l=len(inputs)-1
        prim=inputs[0].split()

    # Evaluate the circuit and find the state of all nets
    for net_id in sorted(g.nodes()):
        print( net_id,end=" ")
    print("\n")
    for j in range (1,l+1):
        input_vector=inputs[j].split()
        # Set the input states of the primary inputs
        states = {}
        for i, input_id in enumerate(prim):
            if g.in_degree(input_id) == 0:
```

```

        states[input_id] = int(input_vector[i])

    # Evaluate the circuit in topological order
    for gate_id in topological_order:
        if g.in_degree(gate_id) > 0:

            input_gate_id=list(g.predecessors(gate_id))
            input_state_list=[states[n] for n in input_gate_id]
            #input_states_list = [states[input_gate_id] for input_gate_id_
↪in list(g.predecessors(gate_id))]
            gate = g.nodes[gate_id]['gate_type']
            states[gate_id] = evaluate_gate(gate, input_state_list)

    # Print the state of all nets
    print(f"Input vector: {input_vector}")
    print("List of states: ",end=" ")
    for net_id, state in sorted(states.items()):
        print(state,end=" ")
    print("\n")
end_time=time.time()
f('c17.inputs')
elapsed_time = end_time - start_time
print(f"Time taken: {elapsed_time:.6f} seconds")

```

N1 N2 N22 N23 N3 N6 N7 n\_0 n\_1 n\_2 n\_3

Input vector: ['0', '1', '0', '0', '0']

List of states: 0 1 1 1 0 0 0 1 1 1 0

Input vector: ['0', '0', '1', '0', '0']

List of states: 0 0 0 0 1 0 0 1 1 1 1

Input vector: ['1', '0', '0', '0', '0']

List of states: 1 0 0 0 0 0 0 1 1 1 1

Input vector: ['0', '0', '1', '1', '1']

List of states: 0 0 0 0 1 1 1 1 0 1 1

Input vector: ['1', '1', '1', '1', '1']

List of states: 1 1 1 0 1 1 1 0 0 1 1

Input vector: ['1', '1', '1', '0', '0']

List of states: 1 1 1 1 1 0 0 0 1 1 0

Input vector: ['1', '1', '1', '1', '0']

List of states: 1 1 1 0 1 1 0 0 0 1 1

Input vector: ['1', '1', '0', '0', '0']

List of states: 1 1 1 1 0 0 0 1 1 1 0

Input vector: ['0', '1', '1', '0', '1']

List of states: 0 1 1 1 1 0 1 1 1 0 0

Input vector: ['0', '0', '1', '1', '0']

List of states: 0 0 0 0 1 1 0 1 0 1 1

Time taken: 0.000764 seconds

**Topologically sorted Evaluation** is a straightforward approach and here we evaluate outputs from level\_1 and move towards the output. It iterates over all the nodes(or nets) every single time.

## 4 Event\_Driven Evaluation:

```
[88]: import networkx as nx
import time
start_time = time.time()
from queue import Queue
filename = "c17.net"
try:
    with open(filename) as f:
        # Create an empty directed acyclic graph (DAG)
        g = nx.DiGraph()
        for line in f:
            parts = line.strip().split()
            if len(parts) < 4:
                raise ValueError("Invalid line: " + line)
            gate_id, gate_type, *inputs, output = parts
            g.add_node(output, gate_type=gate_type)
            for input_node in inputs:
                g.add_edge(input_node, output)
except FileNotFoundError:
    print("Error: File not found:", filename)
    exit(1)
except ValueError as e:
    print("Error:", e)
    exit(1)

# Function to evaluate the logic of a gate
def evaluate_gate(gate_type, input_states_list):
    if gate_type == "and2":
        return int(all(input_states_list))
    elif gate_type == "nand2":
        return int(not all(input_states_list))
    elif gate_type == "or2":
```

```

        return int(any(input_states_list))
    elif gate_type == "nor2":
        return int(not any(input_states_list))
    elif gate_type == "xor2":
        return int(sum(input_states_list) % 2 == 1)
    elif gate_type == "xnor2":
        return int(sum(input_states_list) % 2 == 0)
    elif gate_type == "inv":
        return int(not input_states_list)
    elif gate_type == "buf":
        return int(input_states_list[0])
    else:
        raise ValueError("Invalid gate type")

# Create an empty directed graph

# Read the input values for the primary inputs
with open("c17.inputs") as f:
    inputs = f.readlines()
    l = len(inputs) - 1
    primary_inputs = inputs[0].split()

# Initialize the state of all nets to unknown (-1)
# Create a queue to store nodes whose output state needs to be evaluated

input_vector=inputs[1].split()

queue = []
    # Initialize the queue with primary inputs
for node_id in g.nodes():
    queue.append(node_id)

    # Initialize the states of all gates to None
states = {node_id: None for node_id in g.nodes()}

for node_id in sorted(g.nodes()):
    print(f"{node_id}",end=" ")

print("\n")

for i, input_id in enumerate(primary_inputs):
    states[input_id] = int(input_vector[i])

```

```

    #print(queue)
# Process the nodes in the queue
while queue:
    # Get the next node from the queue
    node_id = queue.pop(0)

    # Check if all input states are available
    if(states[node_id]==1 or states[node_id]==0):
        continue

    input_states_list = [states[input_gate_id] for input_gate_id in g.
    predecessors(node_id)]
    if None in input_states_list:
        # Some input states are not available, so put this node back in the
        queue
        queue.append(node_id)
    else:
        # Evaluate the output state of the gate
        gate = g.nodes[node_id]['gate_type']
        new_state = evaluate_gate(gate, input_states_list)

        # Update the state of the gate
        states[node_id] = new_state

        # Add the successors of the gate to the queue
        for succ_id in g.successors(node_id):
            queue.append(succ_id)

    # Print the state of all nets

print("List of states for input vector 1")
for node_id in sorted(g.nodes):
    print(states[node_id],end=" ")

print("\n")

count=2
for j in range(2,l+1):
    input_vector=inputs[j].split()

    for i, input_id in enumerate(primary_inputs):

        if(states[input_id]!=int(input_vector[i])):
            states[input_id]=int(input_vector[i])
            for succ_id in g.successors(input_id):

```

```

        states[succ_id]=None
        queue.append(succ_id)

    while queue:

        # Get the next node from the queue
        node_id = queue.pop(0)

        # Check if all input states are available
        if (states[node_id]==1 or states[node_id]==0):
            continue

        input_states_list = [states[input_gate_id] for input_gate_id in g.
        ↪predecessors(node_id)]
        if None in input_states_list:
            # Some input states are not available, so put this node back in the
            ↪queue
            queue.append(node_id)
        else:
            # Evaluate the output state of the gate
            gate = g.nodes[node_id]['gate_type']
            new_state = evaluate_gate(gate, input_states_list)

            # Update the state of the gate
            states[node_id] = new_state

            # Add the successors of the gate to the queue
            for succ_id in g.successors(node_id):
                states[succ_id]=None
                queue.append(succ_id)

    print(f"List of states for input vector {count}")
    for node_id in sorted(g.nodes):
        print(states[node_id],end=" ")
    count+=1
    print("\n")
end_time=time.time()
elapsed_time = end_time - start_time
print(f"Time taken: {elapsed_time:.6f} seconds")

```

N1 N2 N22 N23 N3 N6 N7 n\_0 n\_1 n\_2 n\_3

List of states for input vector 1

0 1 1 1 0 0 0 1 1 1 0

List of states for input vector 2

0 0 0 0 1 0 0 1 1 1 1

List of states for input vector 3

1 0 0 0 0 0 0 1 1 1 1

List of states for input vector 4

0 0 0 0 1 1 1 1 0 1 1

List of states for input vector 5

1 1 1 0 1 1 1 0 0 1 1

List of states for input vector 6

1 1 1 1 1 0 0 0 1 1 0

List of states for input vector 7

1 1 1 0 1 1 0 0 0 1 1

List of states for input vector 8

1 1 1 1 0 0 0 1 1 1 0

List of states for input vector 9

0 1 1 1 1 0 1 1 1 0 0

List of states for input vector 10

0 0 0 0 1 1 0 1 0 1 1

Time taken: 0.003223 seconds

**Event\_Driven Evaluation** is not a straightforward method. It iterates over the successors of each input and its successors and the successors of its successors. It won't iterate through every node everytime.

The event-driven simulation approach generally takes less time than the topological sort approach, especially for large circuits with many inputs and gates. In the topological sort approach, the circuit is evaluated in multiple rounds, where each round evaluates the outputs of gates whose inputs are available. This requires repeatedly iterating over the gates and inputs of the circuit, which can be time-consuming for large circuits. Additionally, there may be multiple valid orderings of gates in a given round, which can complicate the implementation of the topological sort algorithm. In contrast, the event-driven simulation approach only evaluates gates when their inputs change, using a priority queue to keep track of the next gate to evaluate. This approach avoids the need for multiple rounds of evaluation and can be more efficient for large circuits with many gates and inputs, especially if many of the inputs do not change frequently. However, the event-driven simulation approach may require more initial setup time to build the priority queue and initialize the state of the circuit, compared to the topological sort approach. Additionally, the event-driven simulation approach may be more complex to implement, especially for circuits with complex gate interactions and feedback loops.